

# Introduction to Robotics

## Course no. 1

Andrei Dumitriu

[andrei.dumitriu@fmi.unibuc.ro](mailto:andrei.dumitriu@fmi.unibuc.ro)

Faculty of Mathematics and Computer Science  
University of Bucharest

# About the course: details


- **Grading:**

- 1p laboratory, course and/or relevant extra-curricular activity
- 4p weekly homeworks
- 2.5p project 1: matrix game (bomberman, tetris etc)
- 2.5p project 2: line follower
- 1p: bonus (activities and/or anything extra on the ones above)
- Total: 11p

# Today's agenda


- Arduino - what is it?
- Electrical Current
  - Voltage, Current and Resistance
  - AC vs DC
- Electric components
  - Voltage Source
  - Resistors
  - Capacitors
  - Diodes
- Ohm's law
- Reading a datasheet

# Sense. Analyse. Act.

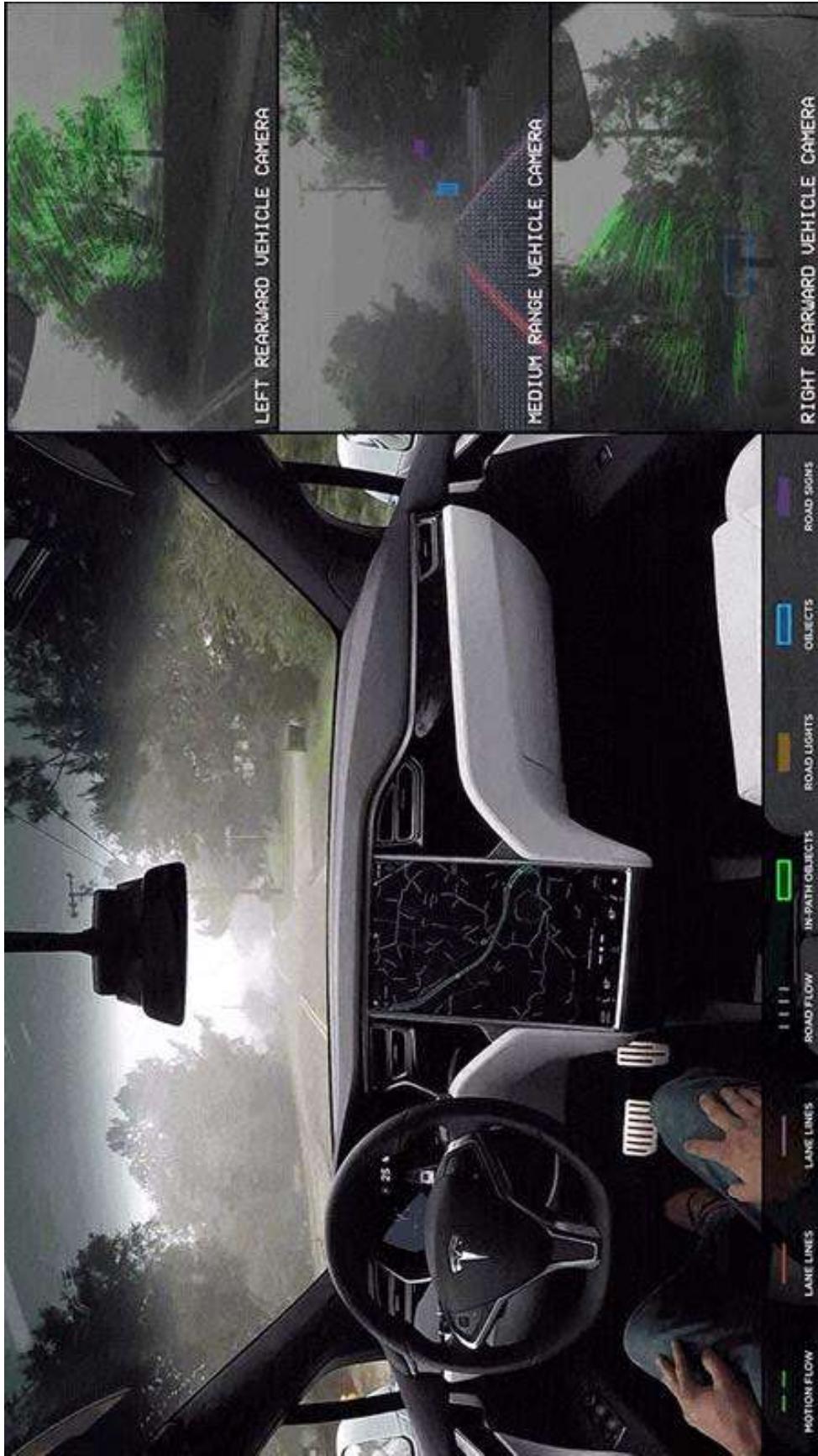


Introduction to Robotics



# Sense. Analyse. Act.

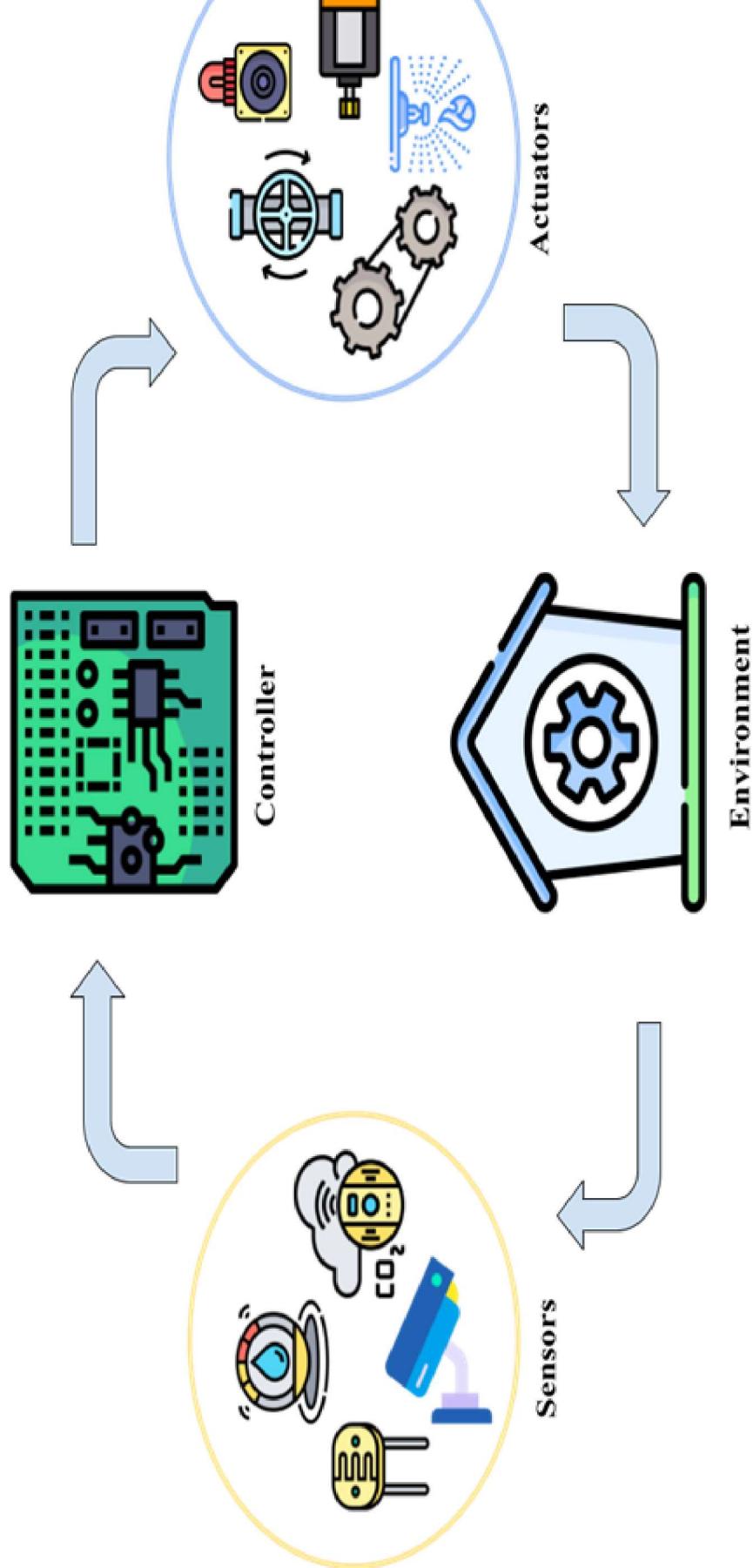

# Arduino Uno board

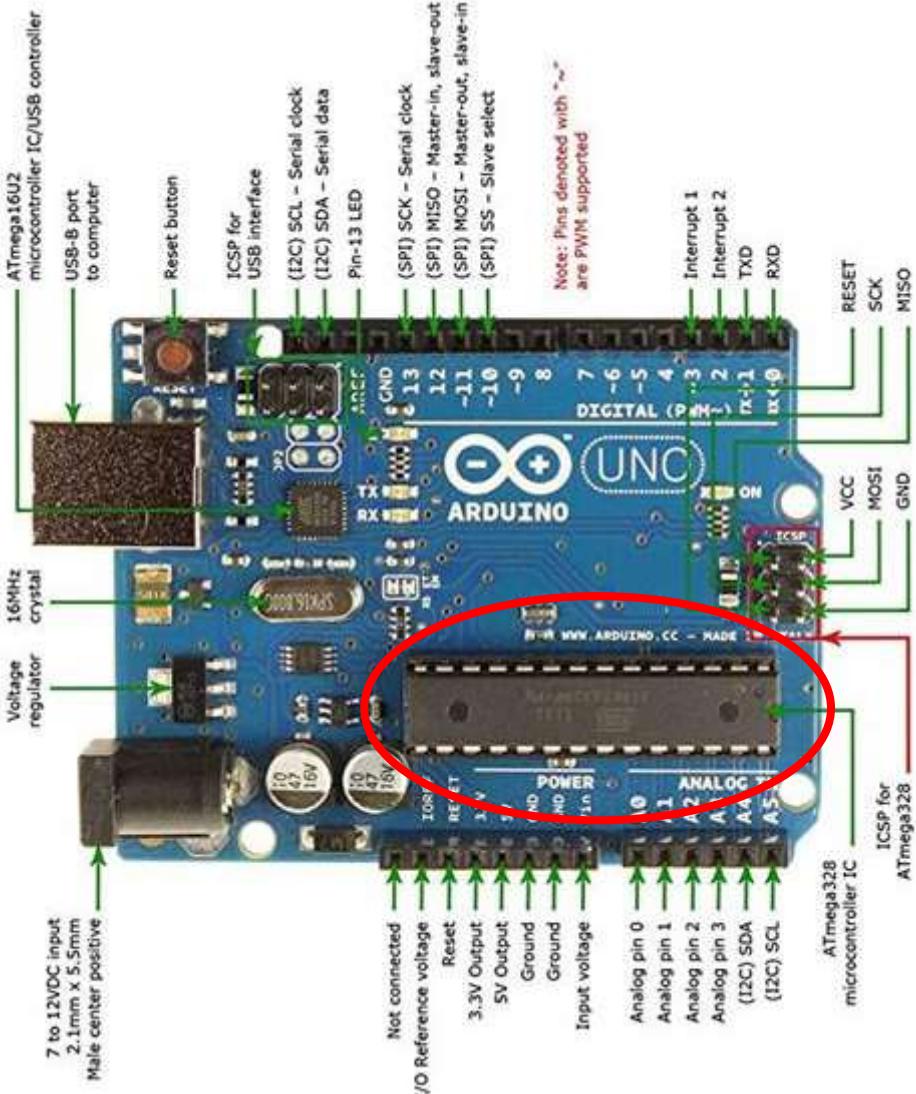

# Arduino Uno board on a breadboard

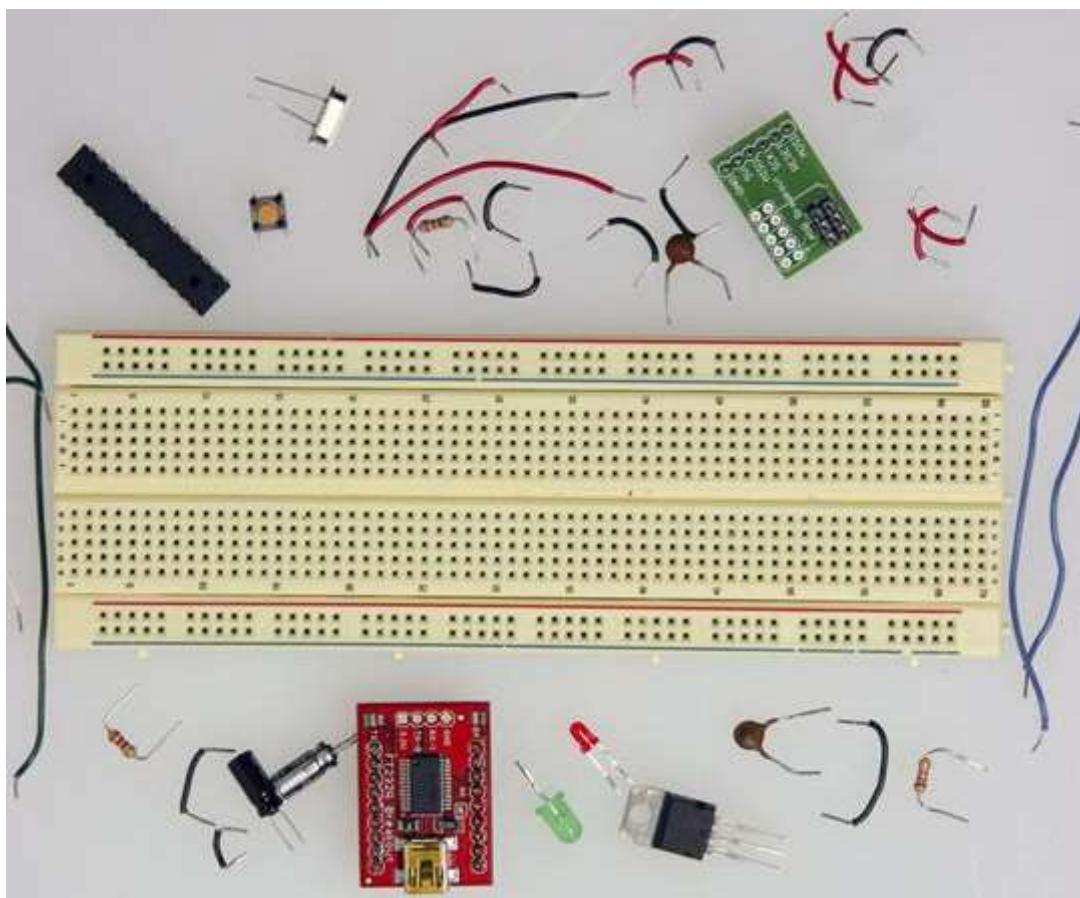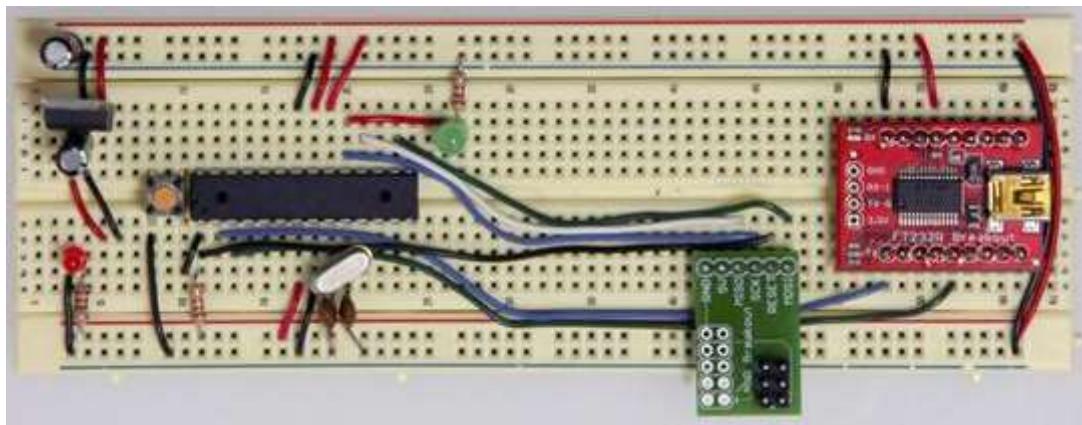

This is a microcontroller  
(AVR ATmega328)



# But what's a microcontroller?

- An integrated circuit
- Basically a tiny computer
- Can run small, simple software programs
- Low power enough to be run on simple batteries for days
- Fast enough to process data efficiently
- A typical microcontroller includes a processor, memory and input/output (I/O) peripherals on a single chip


# WARNING

We will work with the **HIGH-LEVEL concepts** and integrated circuits.

It is not our purpose to design IC, but to understand:

- how to select an IC
- how to connect an IC
- how to understand its limits
- how to use its capabilities

## Introduction to Robotics

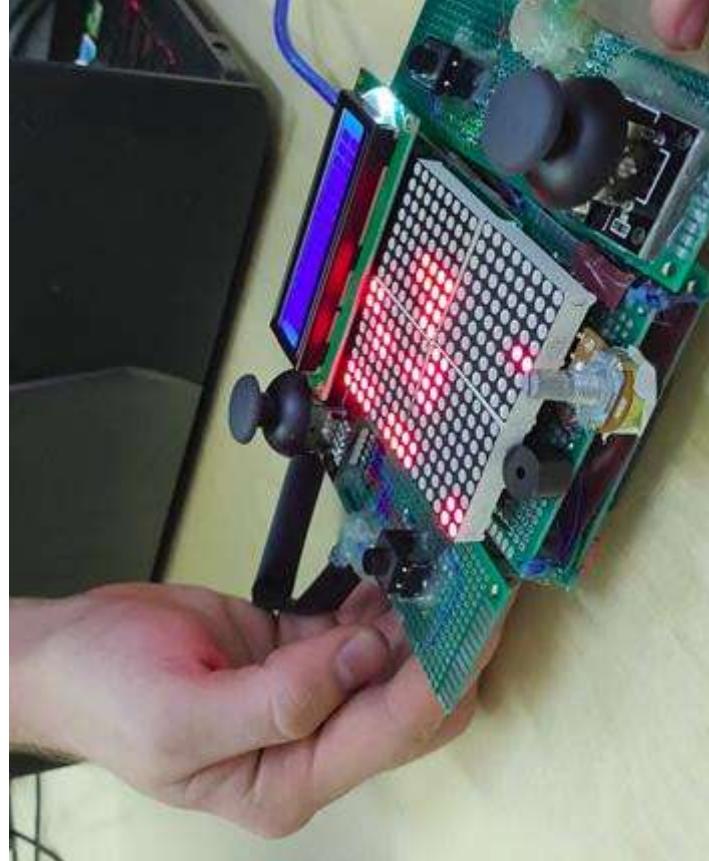


# Electric Current

Before you understanding those, though, you need to understand fundamentals, starting with the electrical current.

**Electric circuit:** a closed loop that carries electricity.

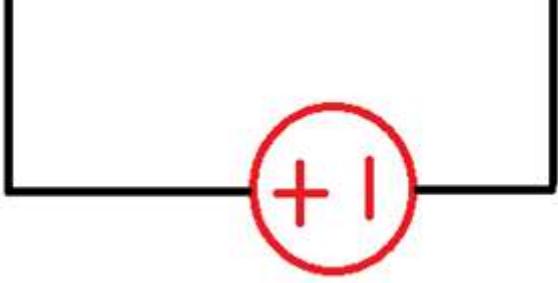Picture on the right is correct, but what's wrong with it?




<https://www.youtube.com/watch?v=gYvXlv7Sj3s>

# Electric circuit

Before you understanding those, though, you need to understand fundamentals, starting with the electrical current.


**Electric circuit:** a closed loop that carries electricity.

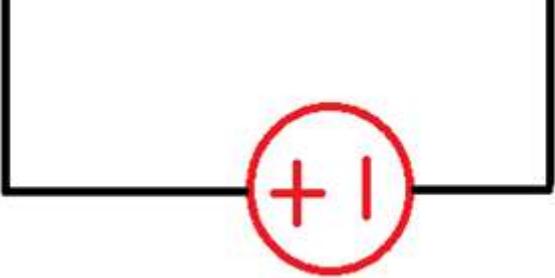Picture on the right is correct, but what's wrong with it?



In a circuit like this there is no resistance, which can cause overheating and even fire.  
Usually there is a consumer in the circuit.

# Current, Voltage and Resistance

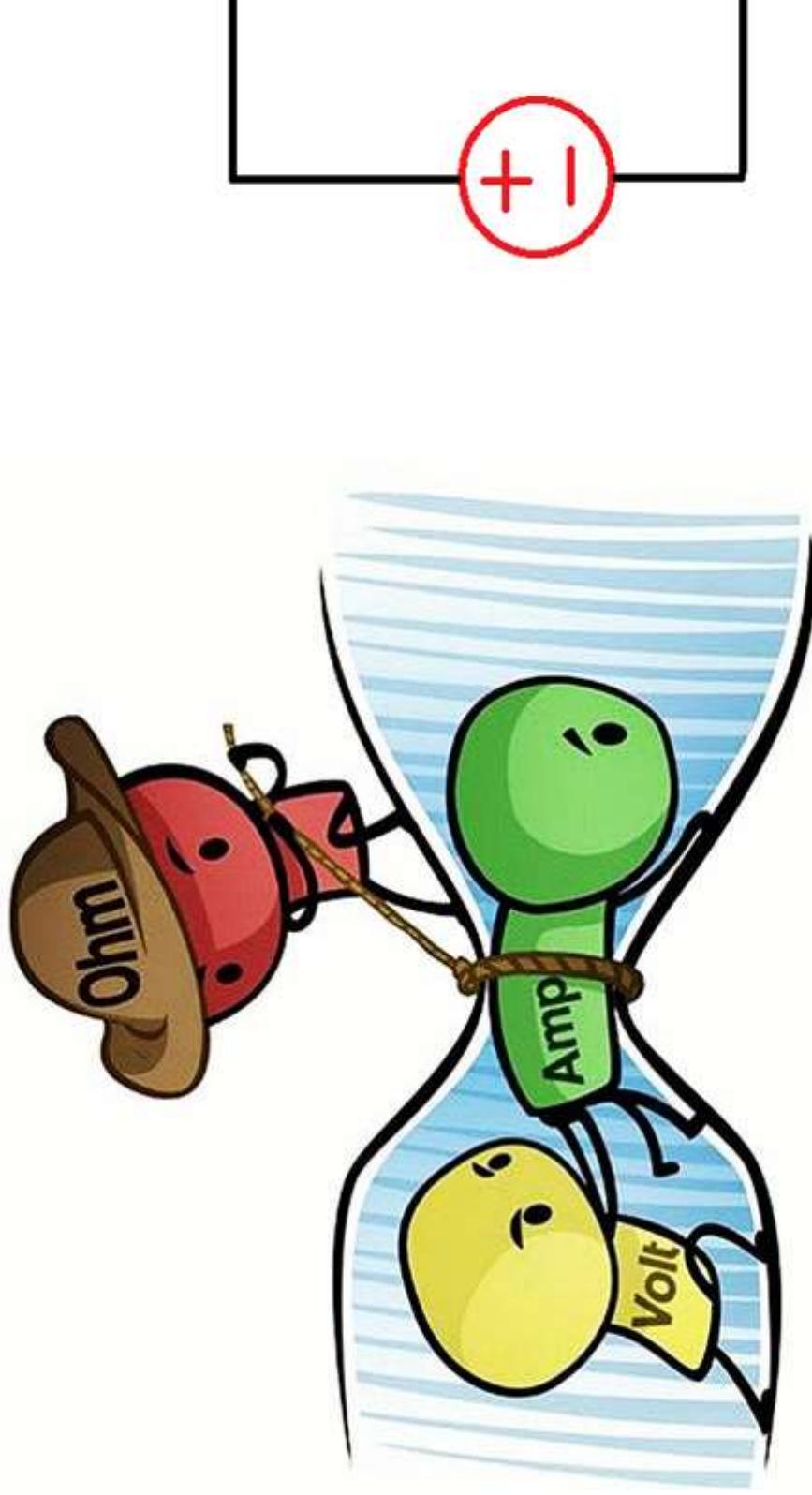

# Electric Current


**Electric current:** flow of electrons in a circuit.

It is the **movement**, do not confuse it with voltage.

Some analogies include a water current that moves the boat or a wind current that pushes the sail.


Why do electrons “jump” from one atom to the other?

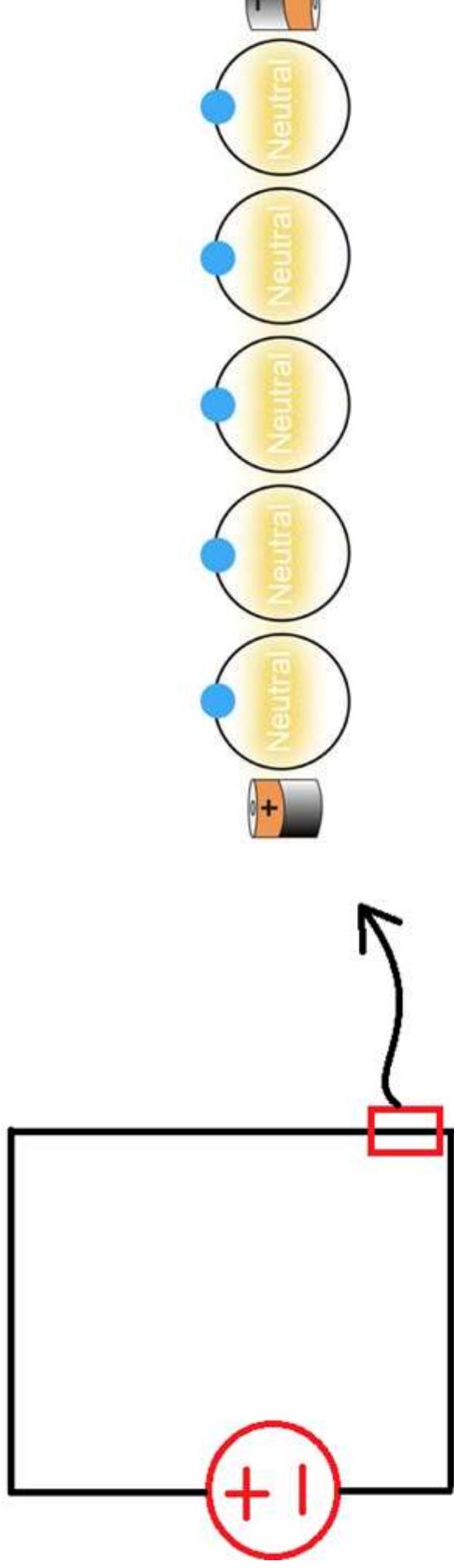- Basically, it's the potential (the voltage) that pushes the electrons. Each ion (positively charged atom) attracts a new ion. We'll leave some info for diving deeper.


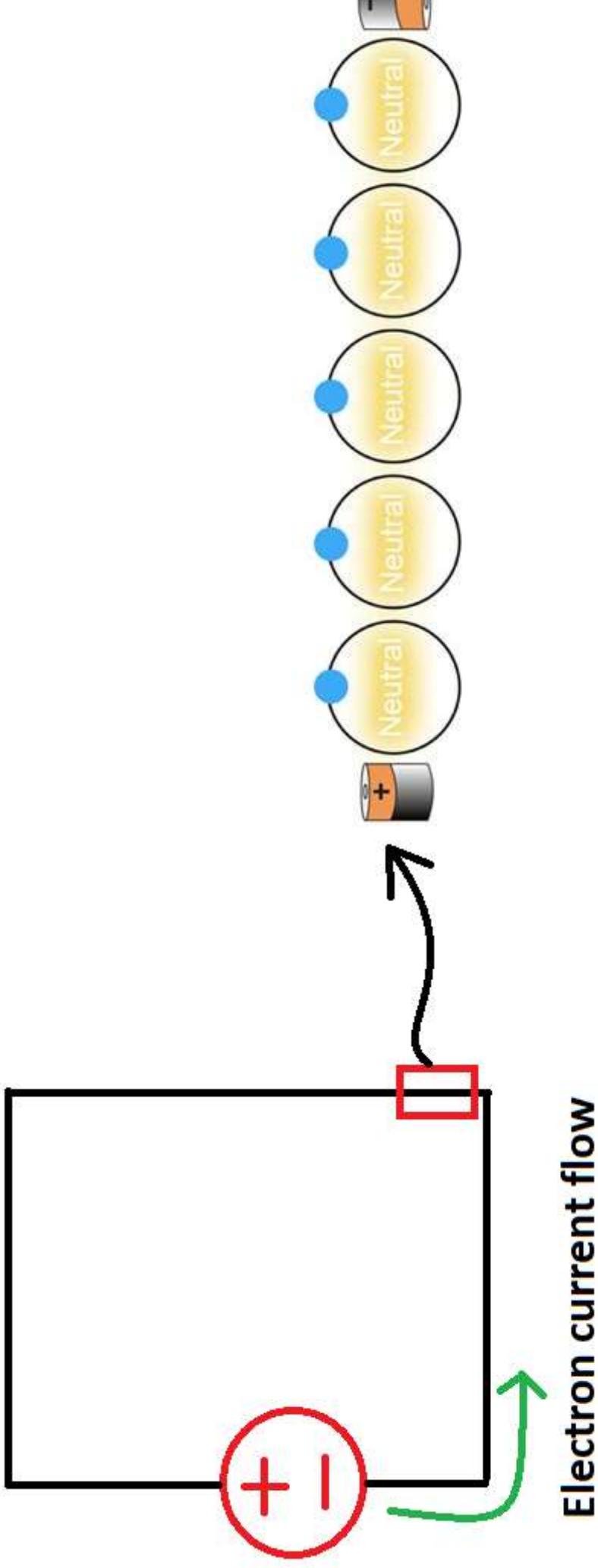
# Electric Current


Understanding the difference between conventional electric current flow because it leaves a “hole” behind) and electron current flow.  
Reasons vary from historic decisions and not wanting to have a lot of “-” in


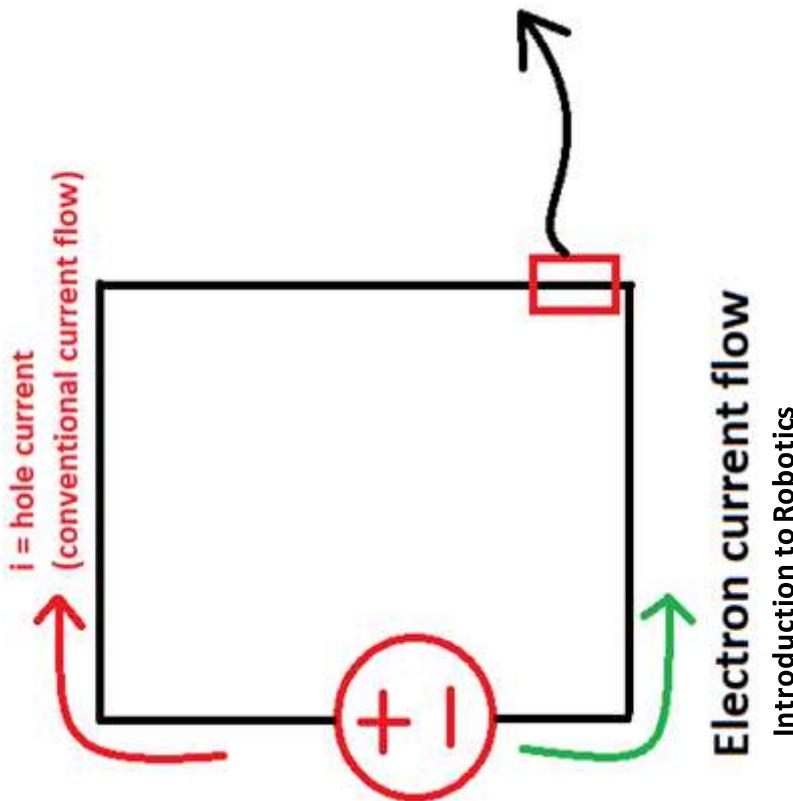
# Electric Current


Imagine instead of seeing the electrons (thus, the negative charge) moving from minus to say - and it would be mathematically correct - that the positive charge moves from plus to

We will be working with conventional current flow.



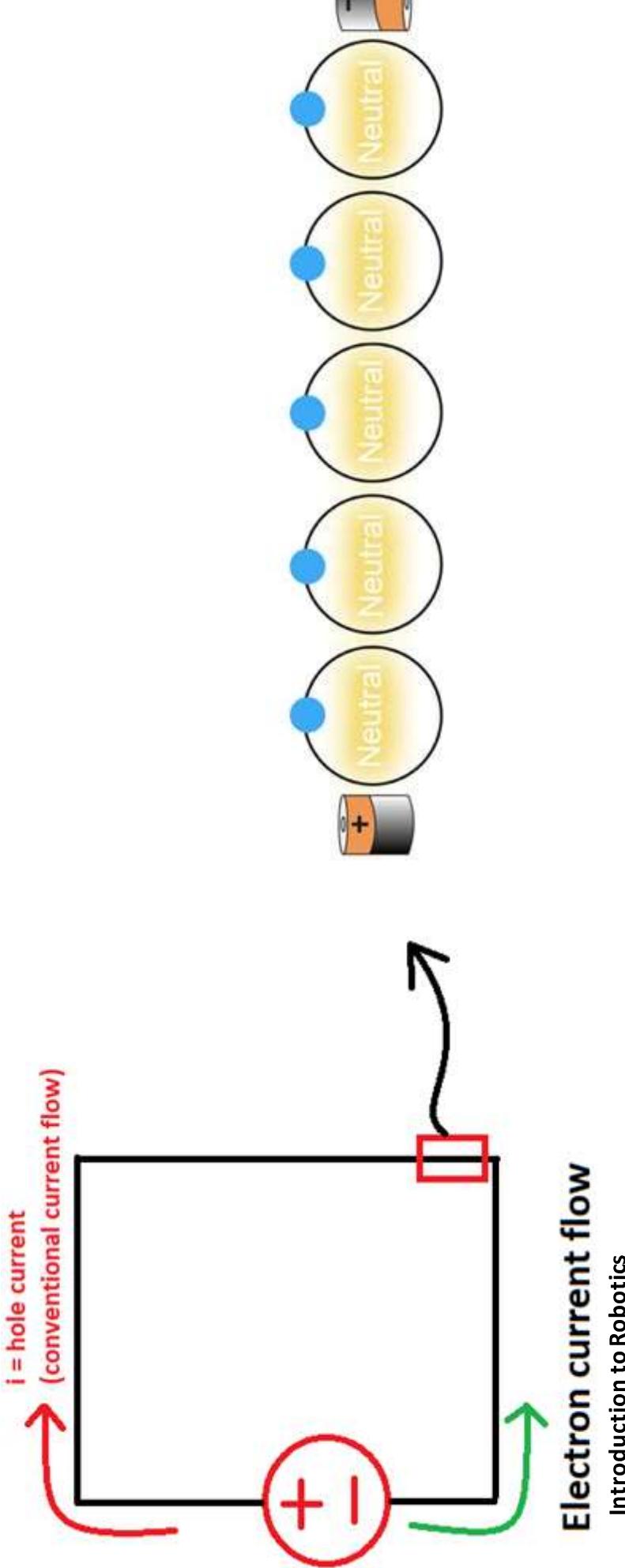
# Electric Current

This is all very basic, yet super important concept. Take a moment to internalize it. **All the calculations are done using hole current**, even though the electrons are moving from minus to plus.


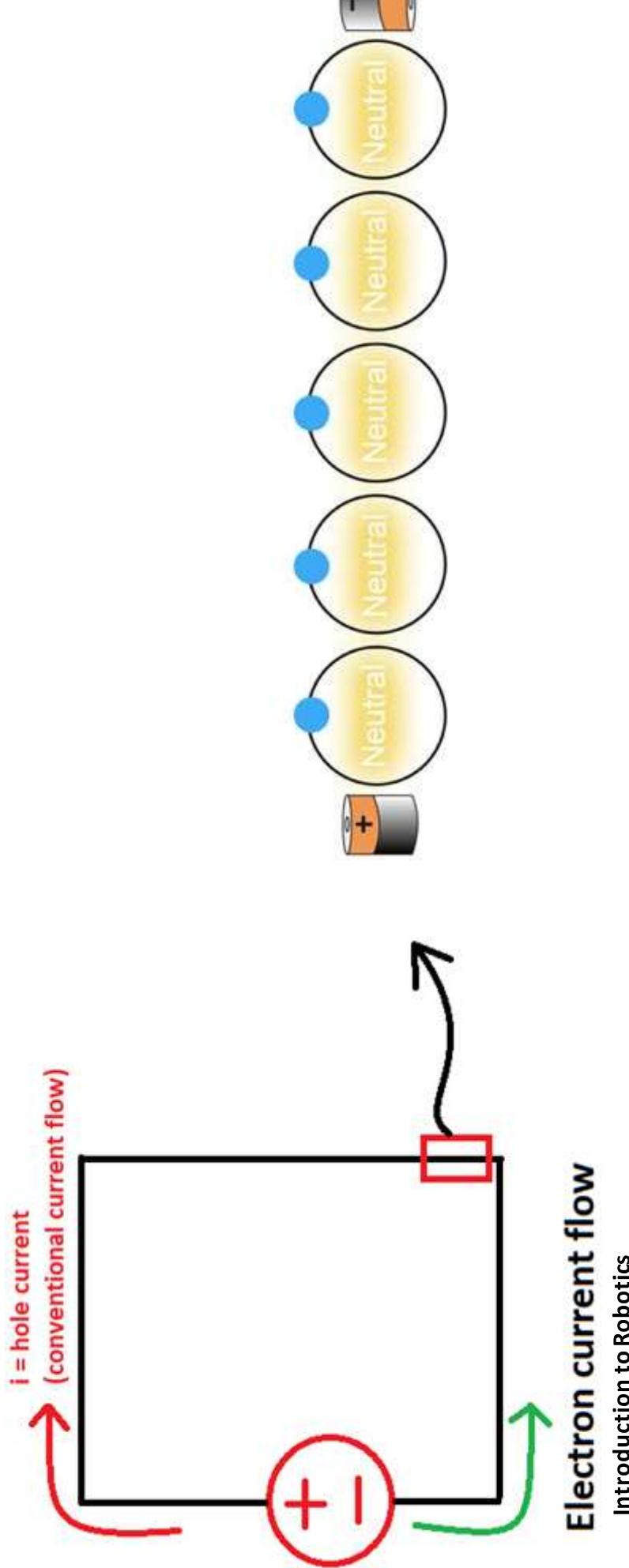
# Electric Current

Units = Ampere (Amp, or “A”).  
We will be working with millamps (mA)  
Amps is the stuff that kills you.



# Electric Current

To sum it up:

- current in real life is the flow of electrons
- in all circuits we're not gonna talk about that
- we're gonna say that current comes out the positive terminal  
the unit of measure is the ampere.

# Voltage

**Do not confuse with current.**

**Voltage = the “push” that causes current to flow.**

You cannot have any current flowing without something to push  
When you see that “you can be killed by 10000 volts” it’s incorrect  
The current kills you, the voltage only causes that current.

Think of blowing through a straw. The air movement is the current  
pressure is the voltage. (can you guess which is resistance?)

# Voltage

**Do not confuse with current.**

**Voltage** = the “push” that causes current to flow.

Units = Volt (V)

We will be working mostly with 5V, but generally with an interval  
3.3V and 12V.

# Resistance


**It opposes the current flow in a circuit.**

Think about the straw. What happens if you increase or decrease diameter?

Units = Ohm ( $\Omega$ )

We will be working with units from 110 ohms to few thousand ohms.

# Current, Voltage and Resistance

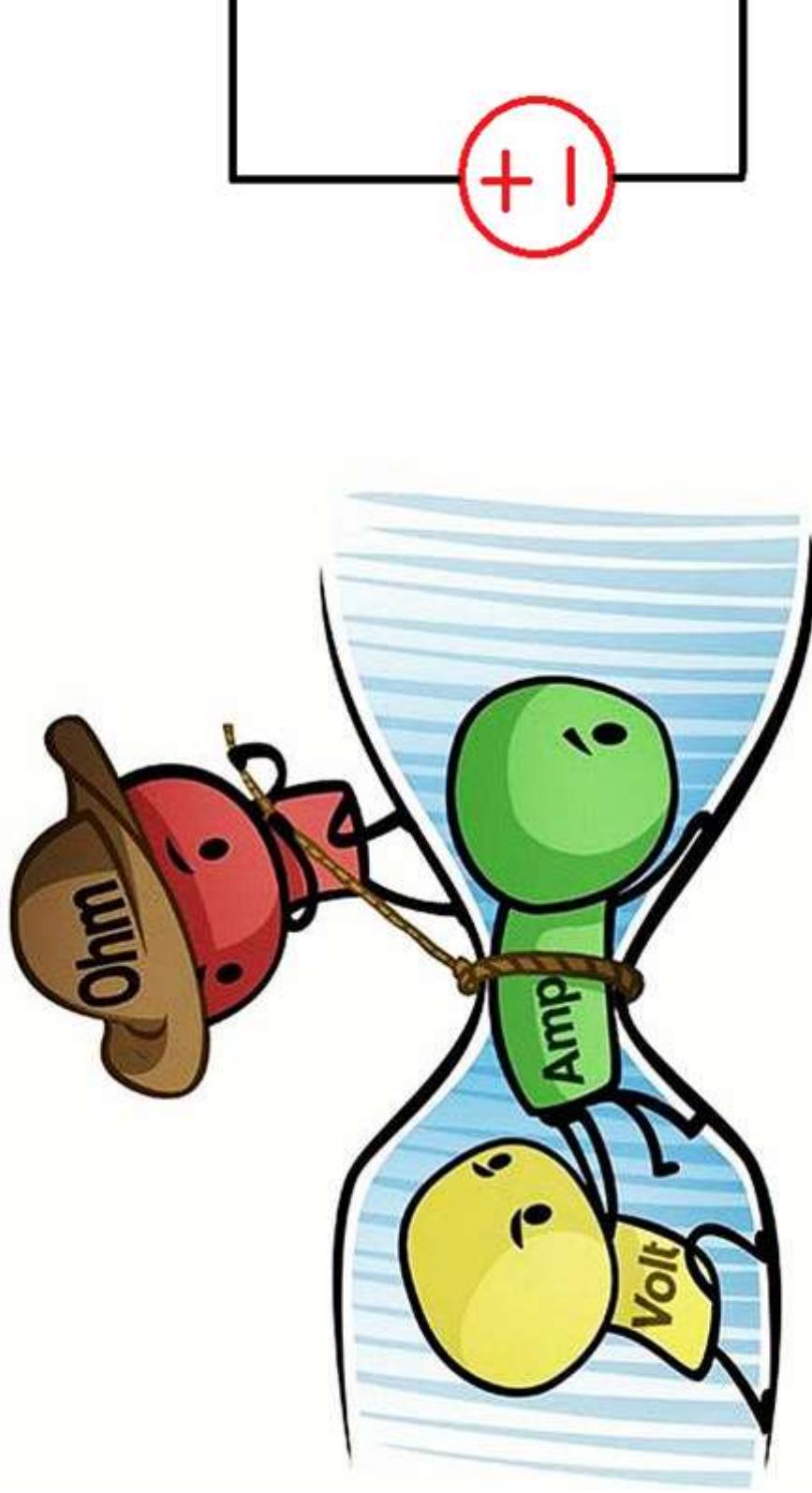



**AC - Alternating Current** - Current moves back and forth.  
The wall sockets that you use have alternating current.

**DC - Direct Current** - Constant current flow.



All the batteries you used generate direct current. It gives you constant voltage at the source location (in reality, the battery does die down current gets weaker, but in a snapshot it's constant).

# AC



The sine wave is the most common waveform for AC, but not the only one.

<https://www.youtube.com/watch?v=WhATiUHgzxQ>



Alternating Current: The Water Analogy

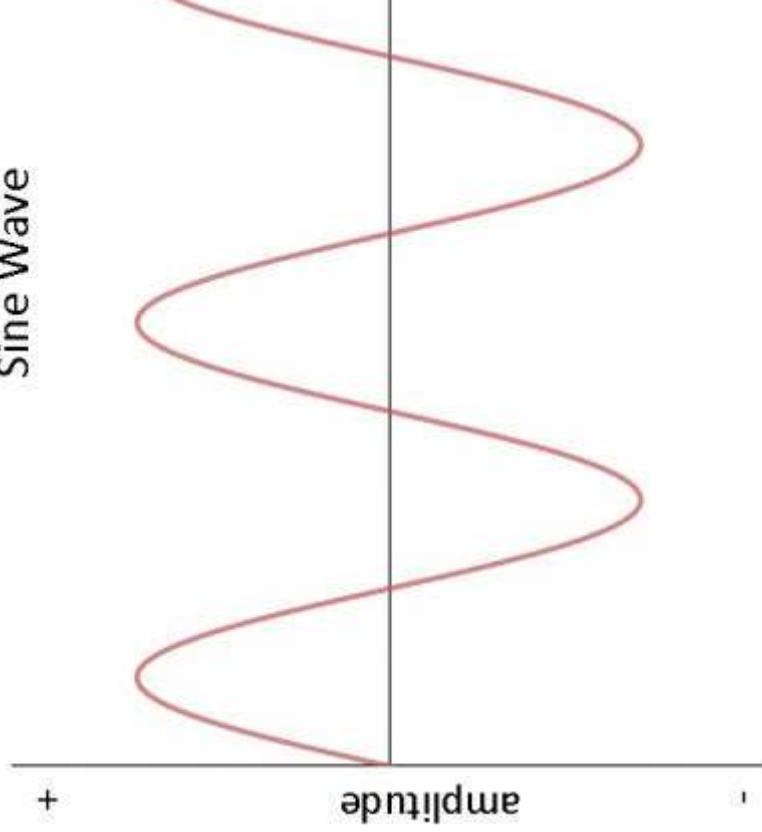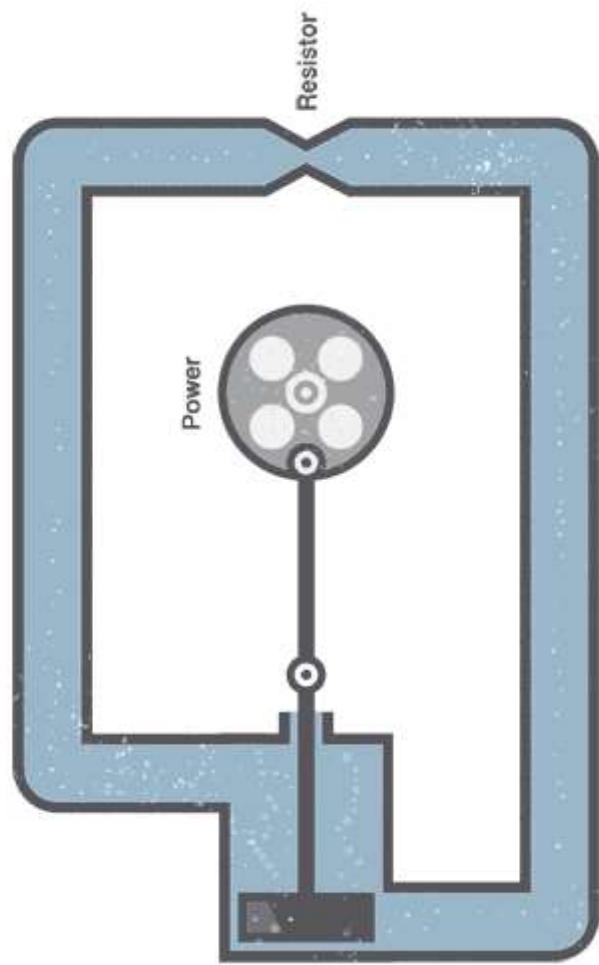

# DC

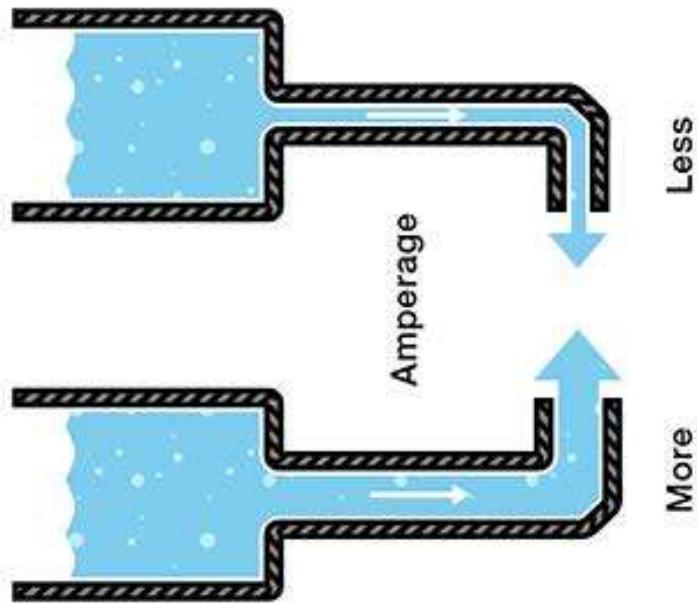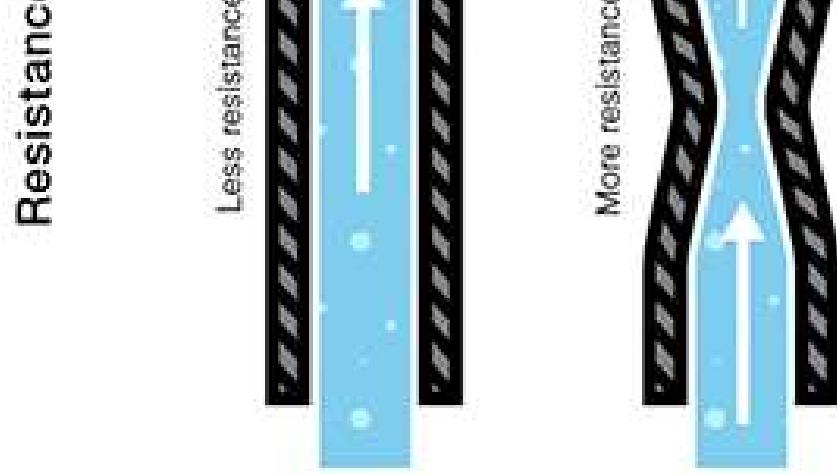

# DC

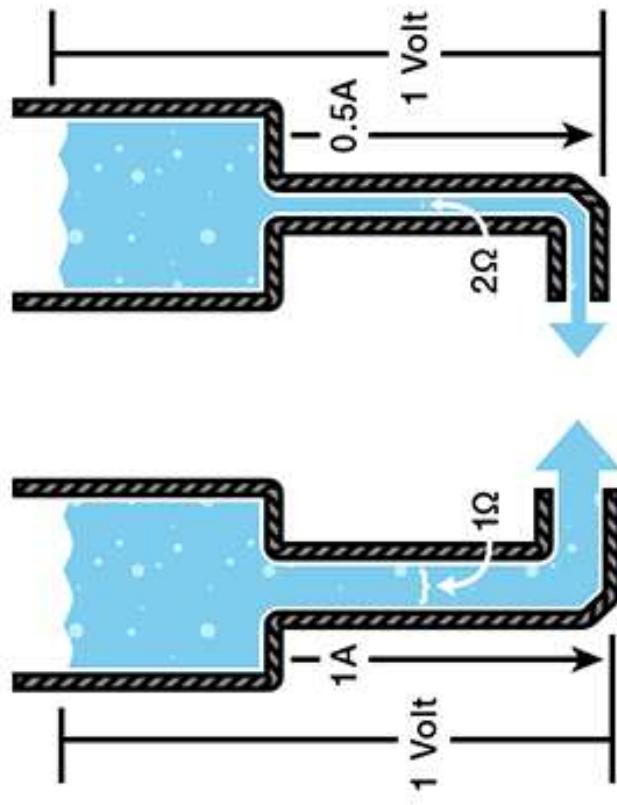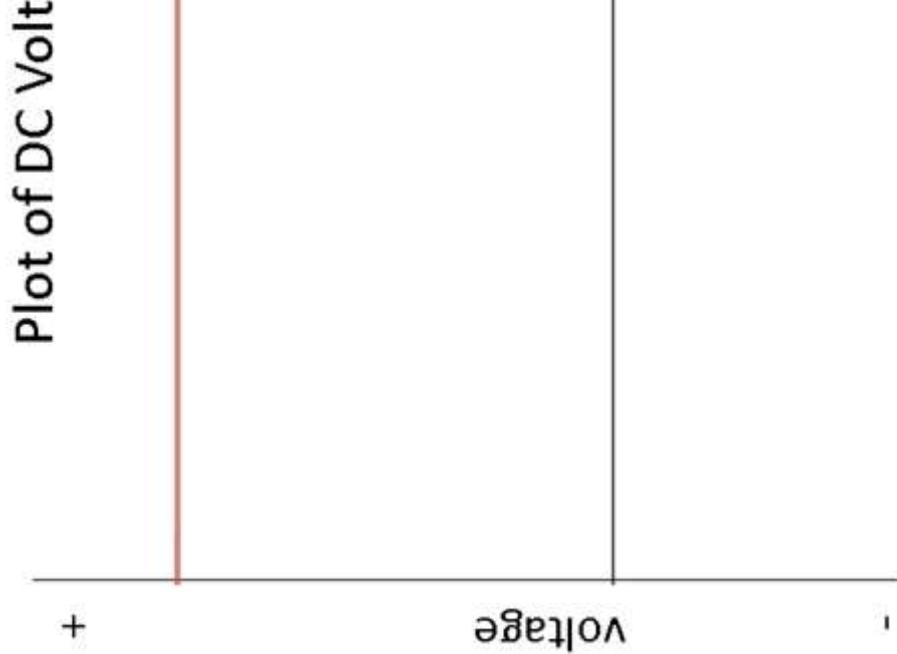

# AC/DC

The choice for AC over DC in households has been due to AC being transported over long distances.


It's also easier to generate at power plants etc since they generate steam and moves a generator. The wind farms work. Exceptions are batteries, that have a chemical reaction, and solar. These generate direct current.

We will not be directly using AC in this course.

**Q:** why isn't the light flickering in the house since you use AC?

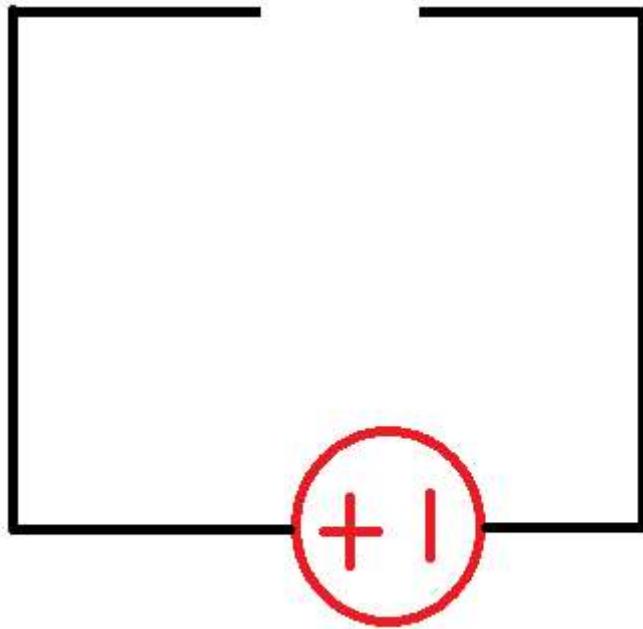
# Open Circuit

An interrupted circuit through which current does not flow.



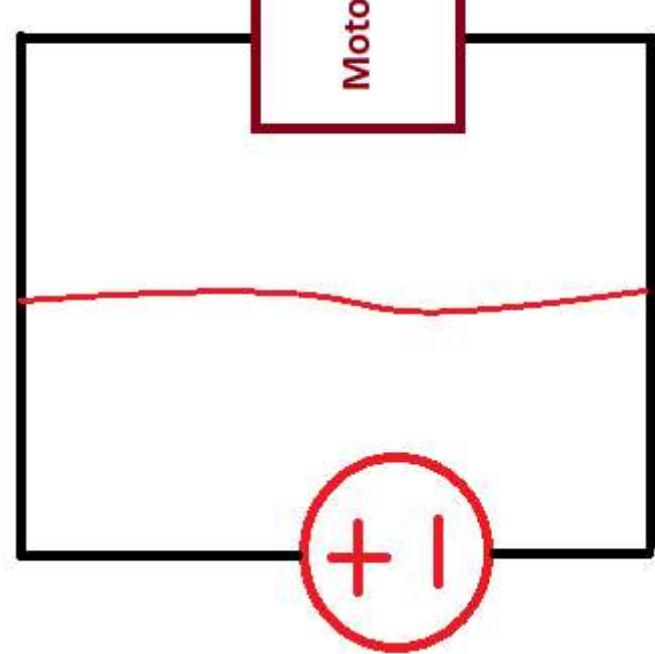
# Short Circuit

When you have a circuit with a consumer, but inside it a piece of accidentally connects to two terminals (parts of the circuit).  
What do you think will happen?


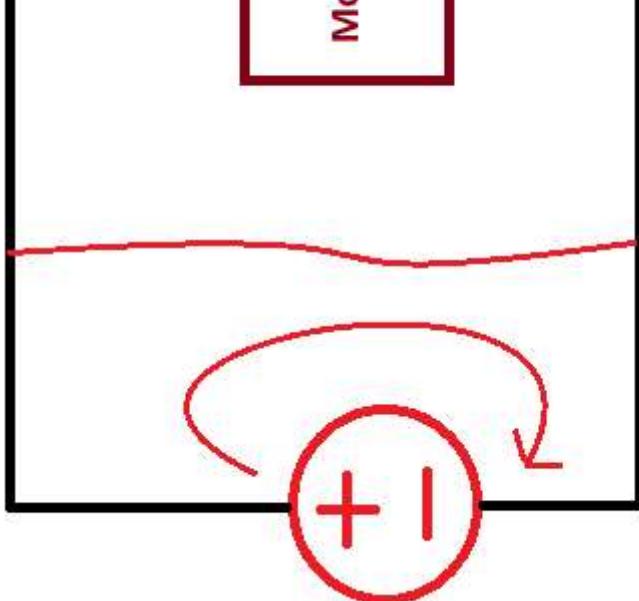
# Short Circuit

When you have a circuit with a consumer, but inside it a piece of metal accidentally connects to two terminals (parts of the circuit). What do you think will happen?



Remember the foam cutter?

It will generate a lot heat.

And maybe stop the current. Why?

# Electrical Components

You might've heard of them in random conversations.

We'll present a few and look at a big picture overview of what they are.

# Electrical Source

Source Voltage or battery.



Most of the information we'll present is taken from here:

[https://www.electronics-tutorials.ws/dccircuits/voltage-source.](https://www.electronics-tutorials.ws/dccircuits/voltage-source)

# Electrical Source


Source Voltage or battery.

Independent Voltage Sources

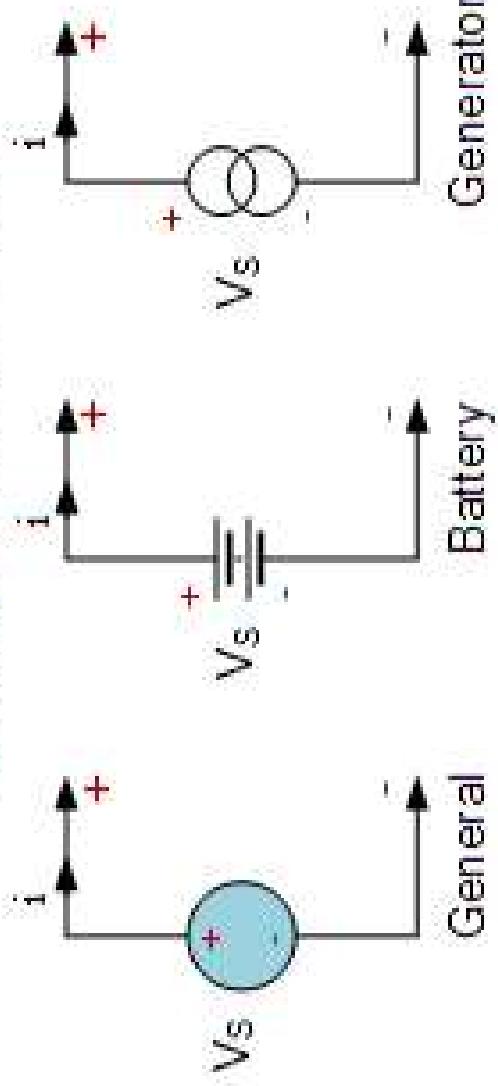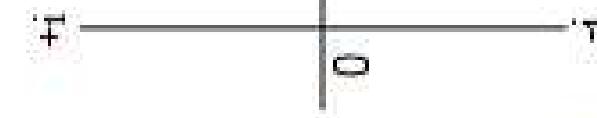


# Electrical Source

## Connecting sources.

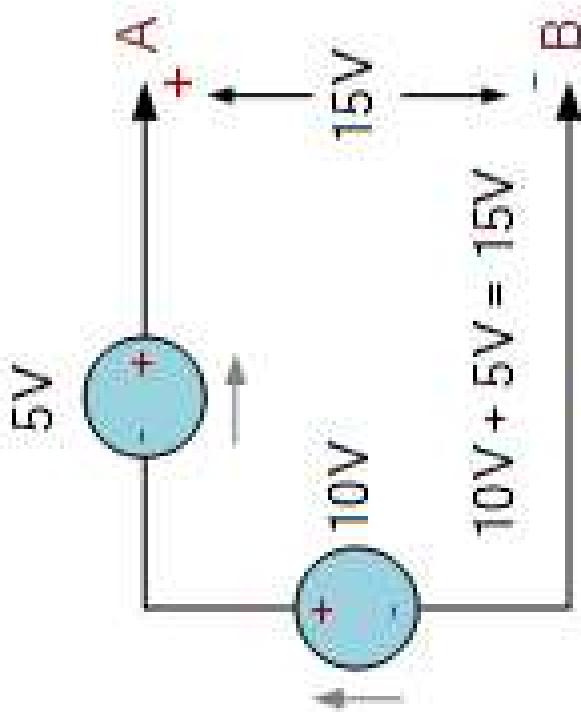

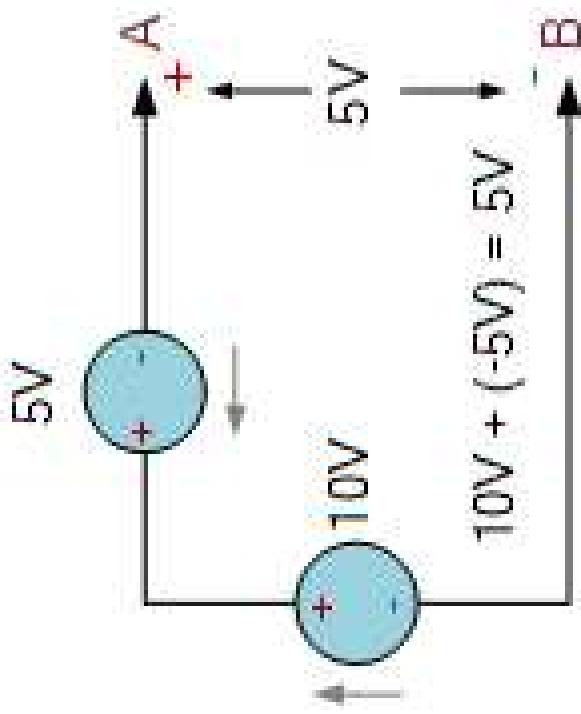
Series Aiding Voltages  
(Voltage Addition)



Series Opposing Voltages  
(Voltage Subtraction)

# Resistor

**JOIN THE RESISTANCE**

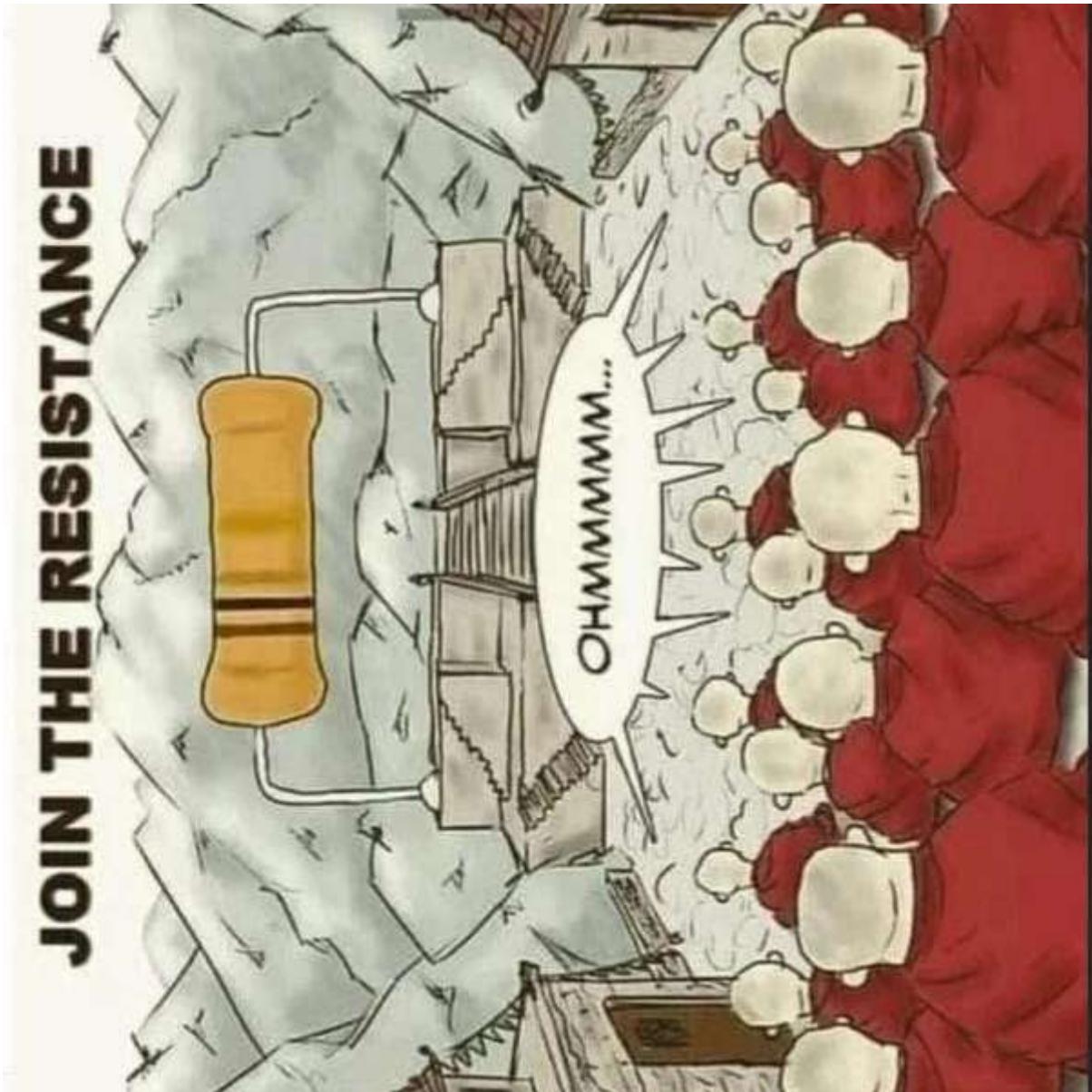


# Rezistor

[https://www.electronics-tutorials.ws/resistor/res\\_1.html](https://www.electronics-tutorials.ws/resistor/res_1.html)

$$R_1 = 100\Omega$$

$$R_1 = 100\Omega$$


or

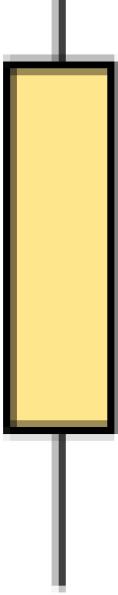

# Resistors

- Electrical components that limit current in a circuit
- Their values can be calculated depending on the color bands
  - There can have, 3, 4, 5 and even 6 color bands, but we'll mostly be with 5. We need to use a table for identifying the value of the colors
    - 1<sup>st</sup> band: 1<sup>st</sup> digit of the value
    - 2<sup>nd</sup> band: 2<sup>nd</sup> digit of the value
    - 3<sup>rd</sup> band: 3<sup>rd</sup> digit of the value
    - 4<sup>th</sup> band: multiplier
    - 5<sup>th</sup> band: tolerance ---- aka, error
    - 6<sup>th</sup> band: temperature coefficient
  - For this course, we can ignore tolerance and temperature coefficient

# Resistor value

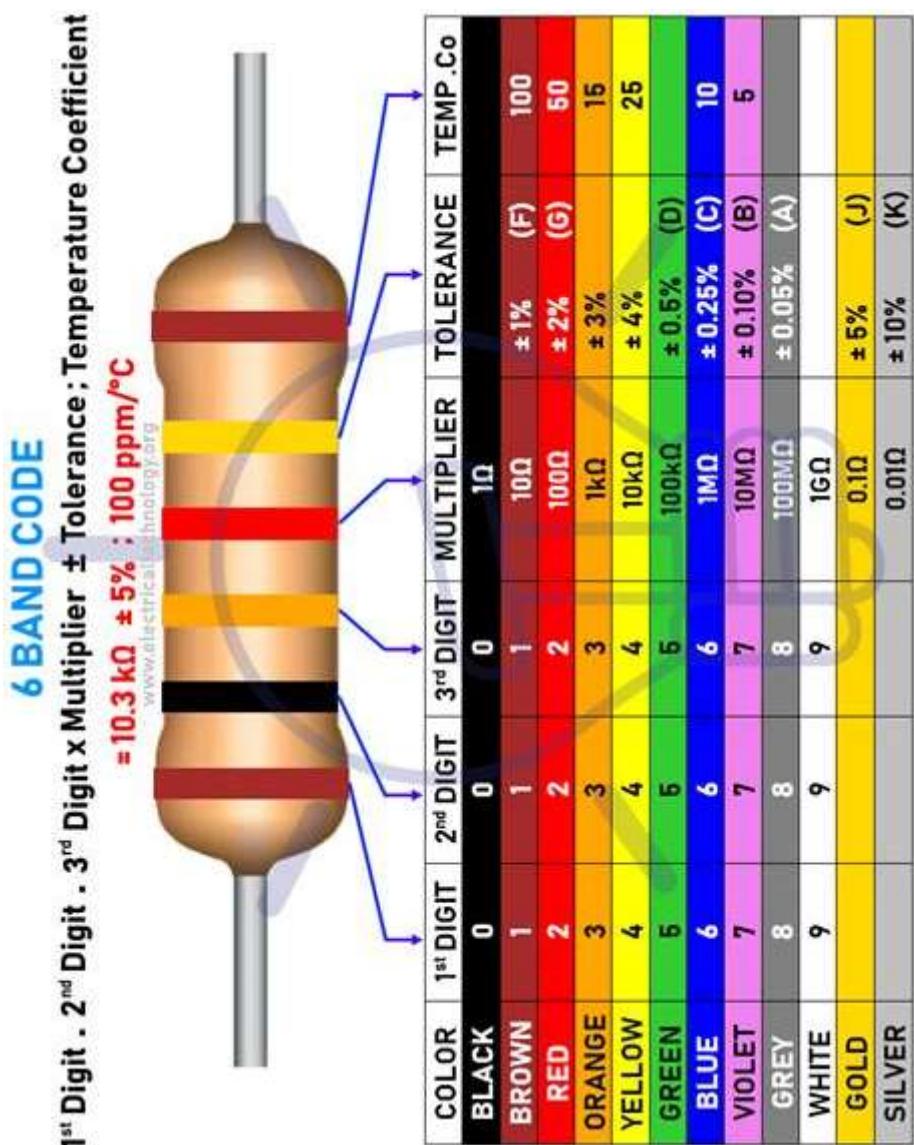

# Resistors

- In order to orient them correctly, pay careful attention to the tolerance ring, as it should be farther apart, but this is not always obvious.
- For cheap and easy to find resistors, the tolerance ring is often gold (5%, 4 band, E12) or red (2%, 5 band, E96)

What value  
have?


# Resistors

- In order to orient them correctly, pay careful attention to the tolerance ring, as it should be farther apart, but this is not always obvious.
- For cheap and easy to find resistors, the tolerance ring is often gold (5%, 4 band, E12) or red (2%, 5 band, E96)

A 2260Ω, 1 with 5 color from top 2- brown band multiplier (x tolerance. T the tolerance difficult to c

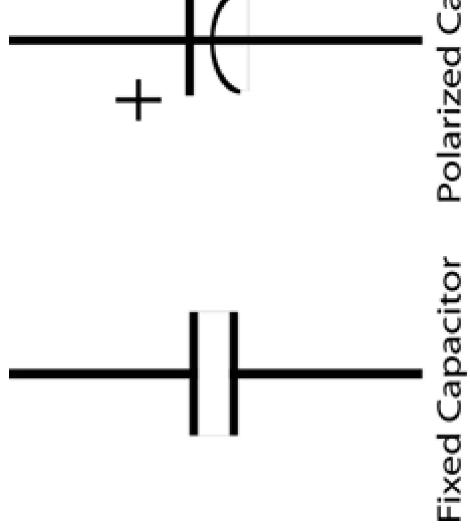
# Capacitor (sau condensator electric)

- [https://www.electronics-tutorials.ws/capacitor/cap\\_1.html](https://www.electronics-tutorials.ws/capacitor/cap_1.html)
  - The capacitor is a component which has the ability or “capacity” to store energy in the form of an electrical charge producing a potential difference (Static Voltage) across its plates, much like a small rechargeable battery.
  - Has faster discharge rate than a battery.
  - Ever heard a blitz charging?



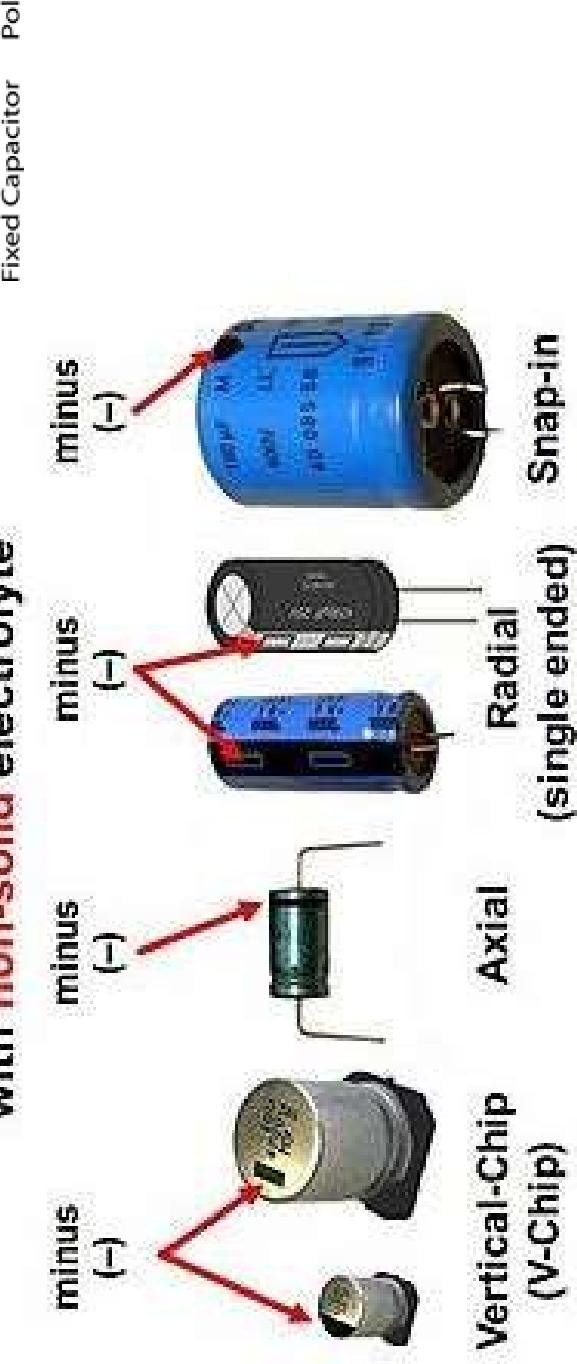
# Capacitor (sau condensator electric)

- Unit = Farad(F)
- 1F is a huge value, we will use  $\mu\text{F}$  usually
- Are used to also absorb noise in a system



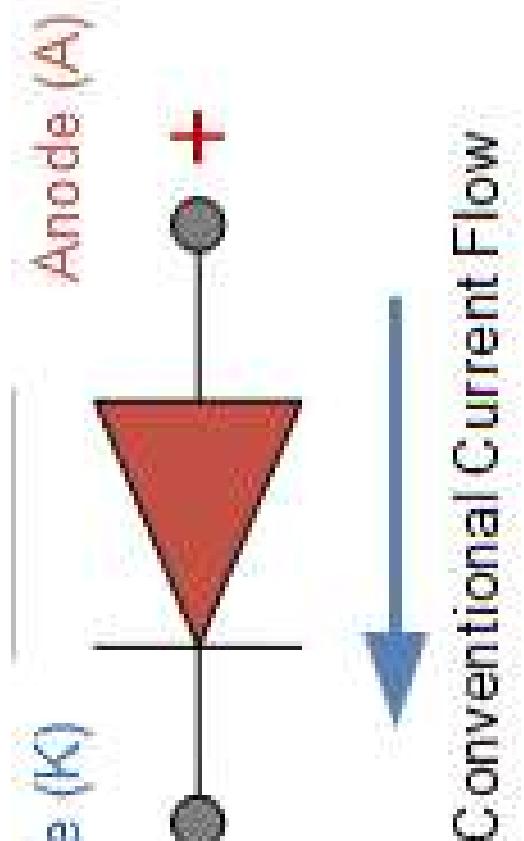
# Diode

- [https://www.electronics-tutorials.ws/diode/diode\\_1.html](https://www.electronics-tutorials.ws/diode/diode_1.html)
- Diodes are basic unidirectional semiconductor devices that allow current to flow through them in one direction only, acting like a one way electrical valve (Forward Biased Condition).
- Can you imagine how such a component would be built?



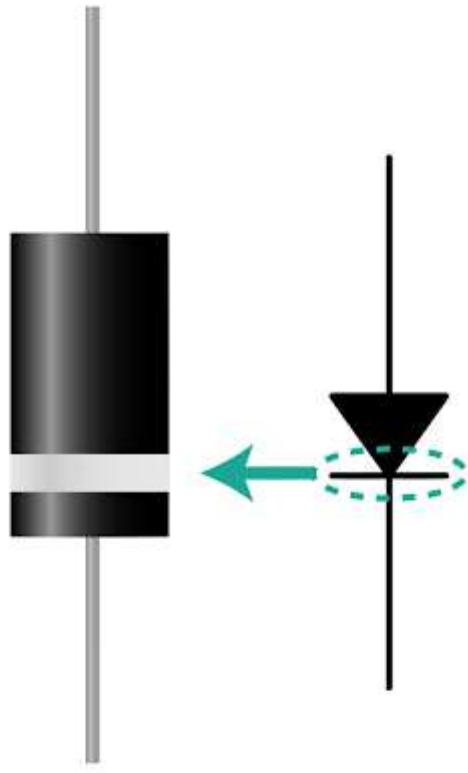
# Diode

- [https://www.electronics-tutorials.ws/diode/diode\\_1.html](https://www.electronics-tutorials.ws/diode/diode_1.html)
- Diodes are basic unidirectional semiconductor devices that will allow current to flow through them in one direction only, acting like a one way electrical valve, (Forward Biased Condition).
- Can you imagine how such a component would be built?



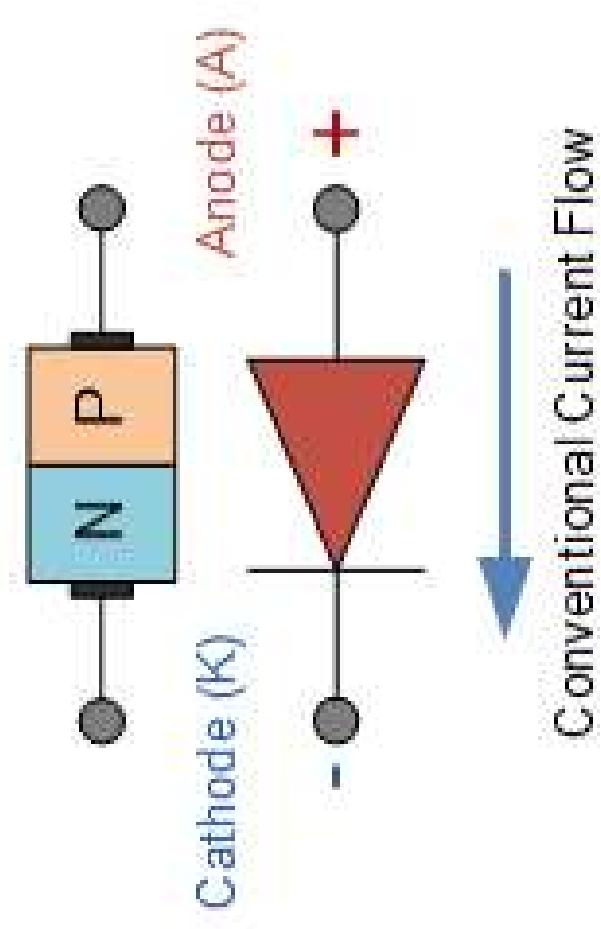
# Diode

- [https://www.electronics-tutorials.ws/diode/diode\\_1.html](https://www.electronics-tutorials.ws/diode/diode_1.html)
- Diodes are basic unidirectional semiconductor devices that allow current to flow through them in one direction only, acting like a one way electrical valve (Forward Biased Condition).
- Can you imagine how such a component would be built?


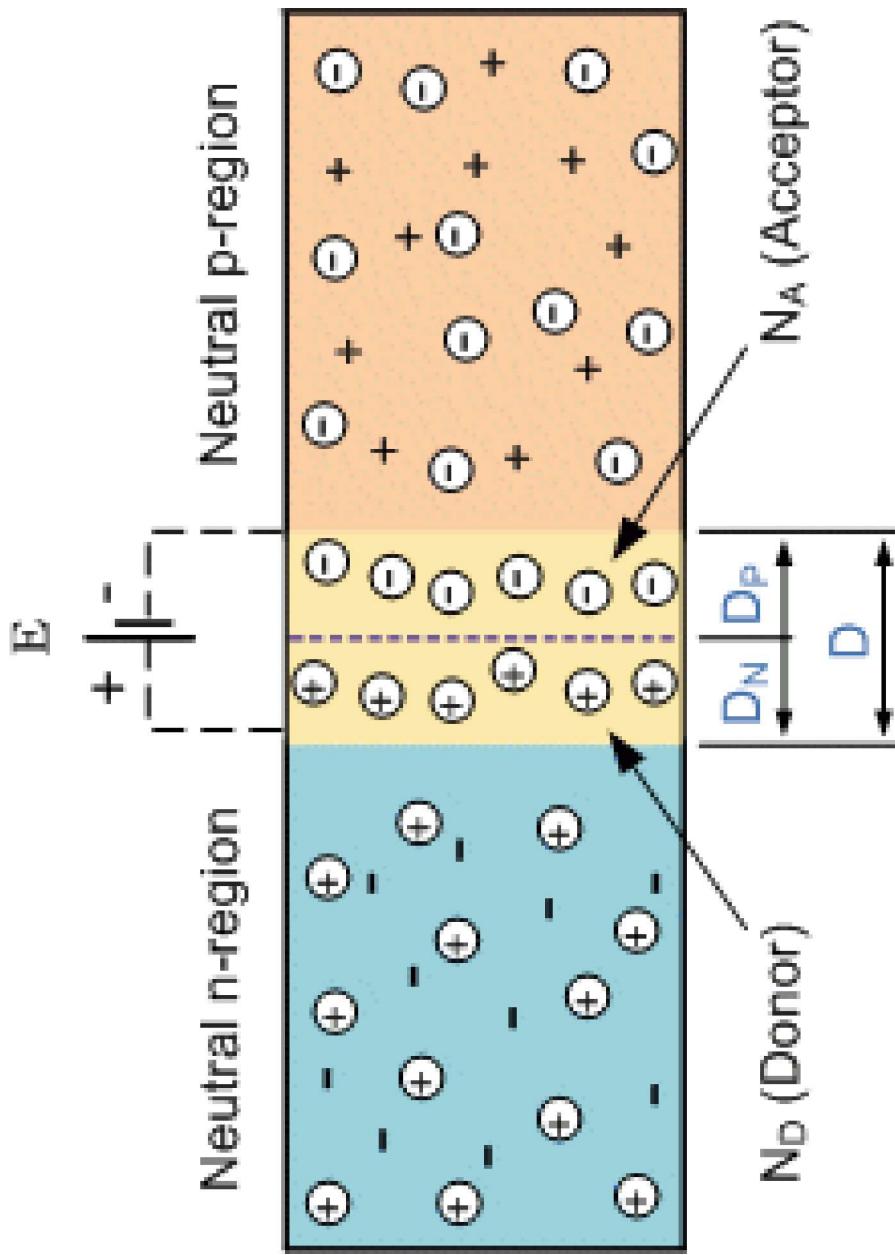
# PN Junction Diode

- [https://www.electronics-tutorials.ws/diode/diode\\_3.html](https://www.electronics-tutorials.ws/diode/diode_3.html)
- More precisely:





- What does it stand for?

# LED
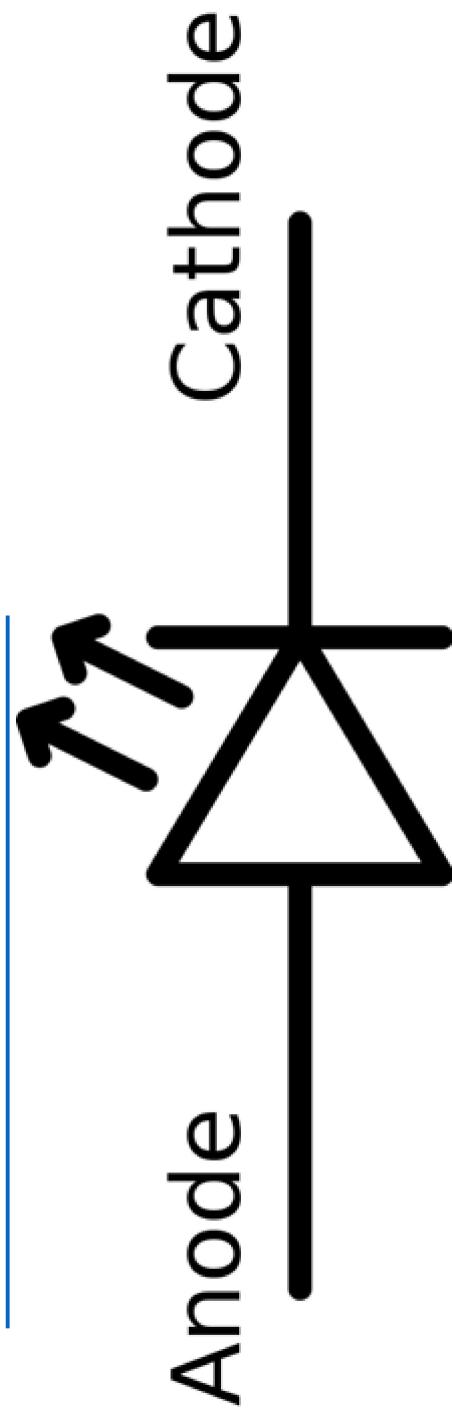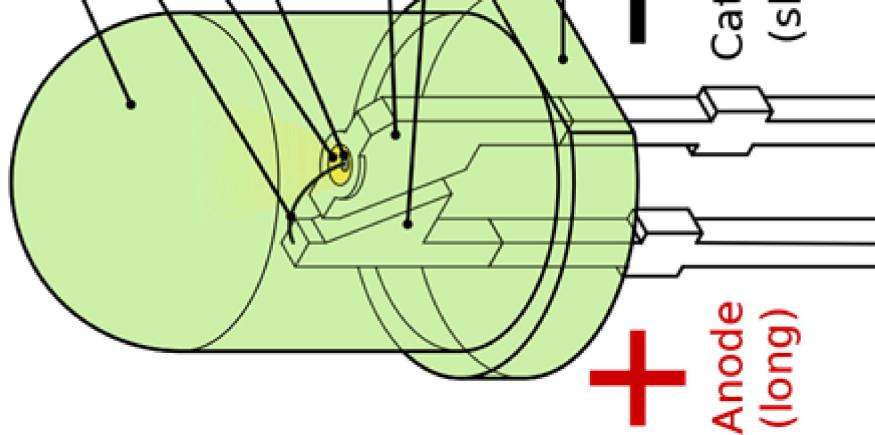
# LED - Light Emitting Diode

- A light-emitting diode (LED) is a semiconductor light source that emits light when current flows through it.
  - Aka a diode that just happens to emit light.
  - The invention of the blue LED won the nobel prize:

<https://www.bbc.com/news/science-environment-29518521>




# Transistor


- Surely you've heard of it.
- Super important.
- Present in pretty much every electrical component.
- Most of the technology in the past 50+ years has been made possible by advancing transistors.
- It's hard to overstate their importance.
- It can do 2 things:
  - Act as an electronic switch with nothing moving inside (main use)
  - Act as an amplifier

# Transistor


PNP Transistor

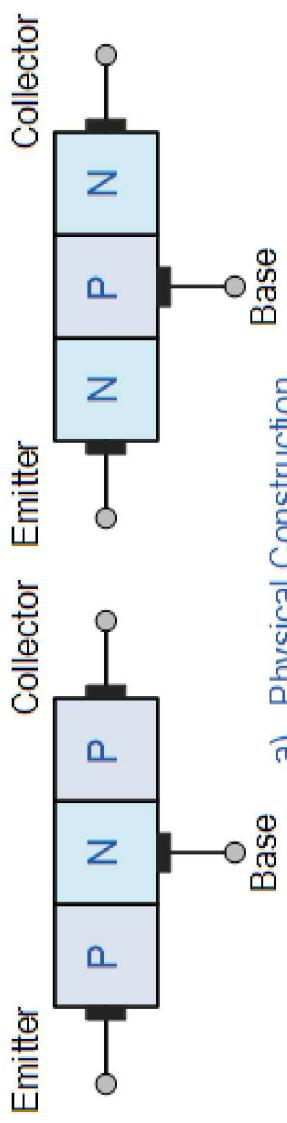

NPN Transistor

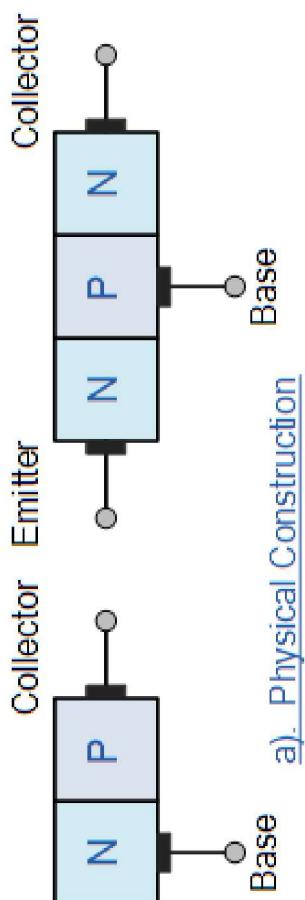

b). Two-diode Analogy

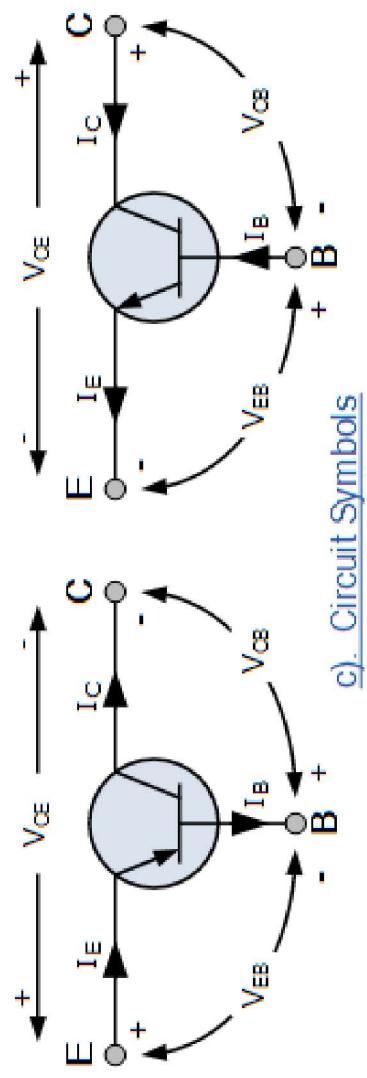

# Transistor


- Take a few million of these and you can do lots of calculation very quickly.
- You basically have a digital binary system.
- They can turn on and off very fast.
- Chips progressed by making transistors faster, smaller and p more on chips (roughly).

# Ohm's Law


- Super simple - super important, serving as a foundation.
- We've talked about:
  - Current being what actually moves in a system.
  - Voltage being what pushes and creates movement.
  - Resistance being whatever is in the way and trying to slow down the movement.
- We are going to look at very simple systems and apply Ohm'
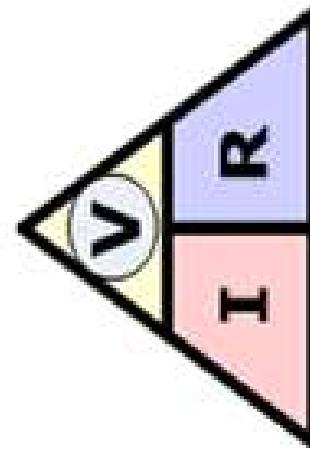
# Ohm's Law


- $V = IR$ 
  - $V \rightarrow$  Voltage (Romanian: U)
  - $I \rightarrow$  Current
  - $R \rightarrow$  Resistance



$$\textcircled{V} = I \times R$$

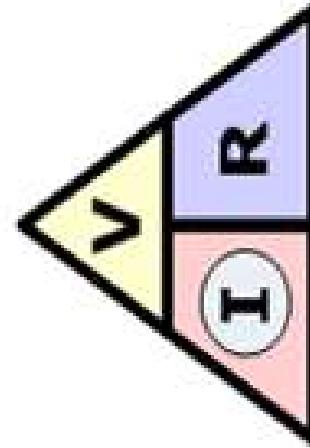


$$\textcircled{I} = \frac{V}{R}$$

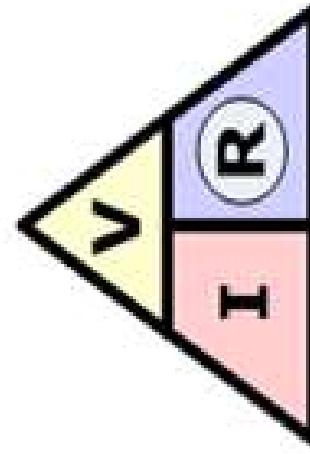

$$\textcircled{R} = \frac{V}{I}$$

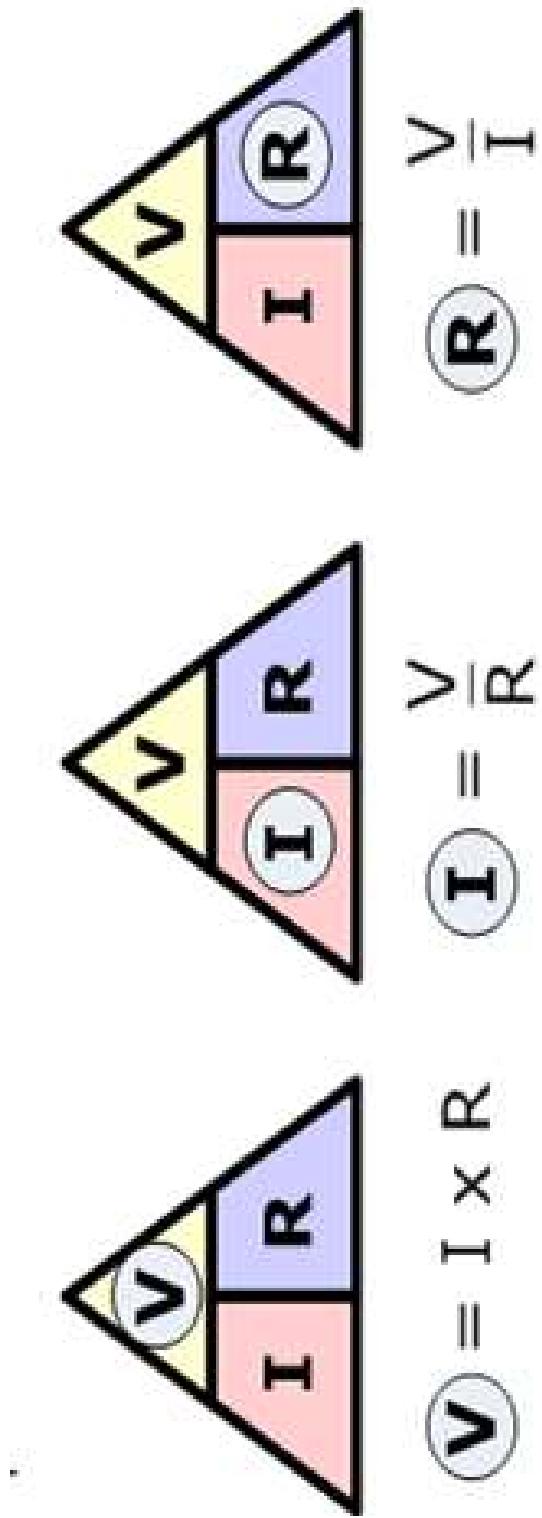
# Ohm's Law

- Think about it logically.  $I = V / R$ 
  - Increasing the voltage increases the current
  - Increasing the resistance decreases the voltage



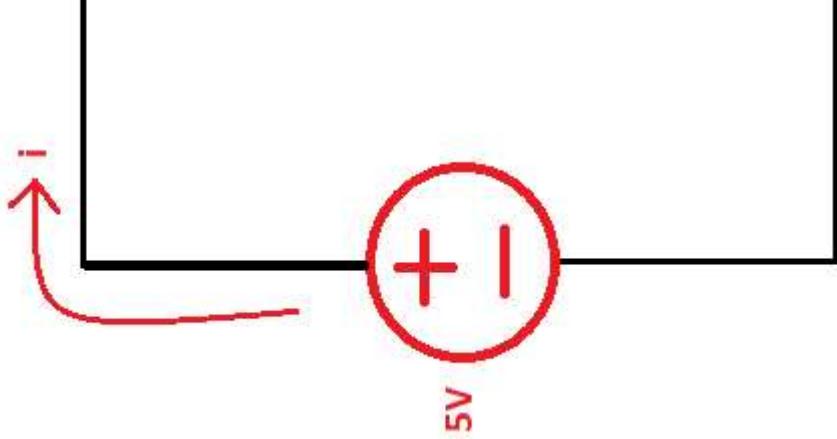
# Ohm's Law

- Some simple examples
- What's the current here?



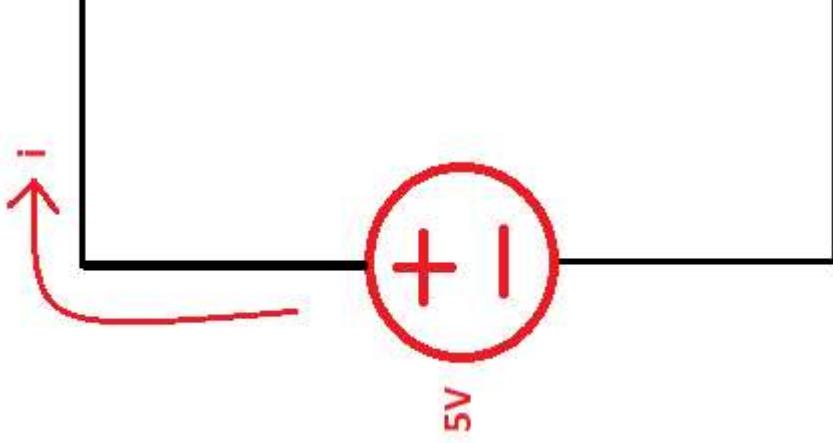
# Ohm's Law

- Some simple examples
- What's the current here?
- $I = V / R \rightarrow I = 5V / 2\Omega \rightarrow I = 2.5 A$  (quite a lot)


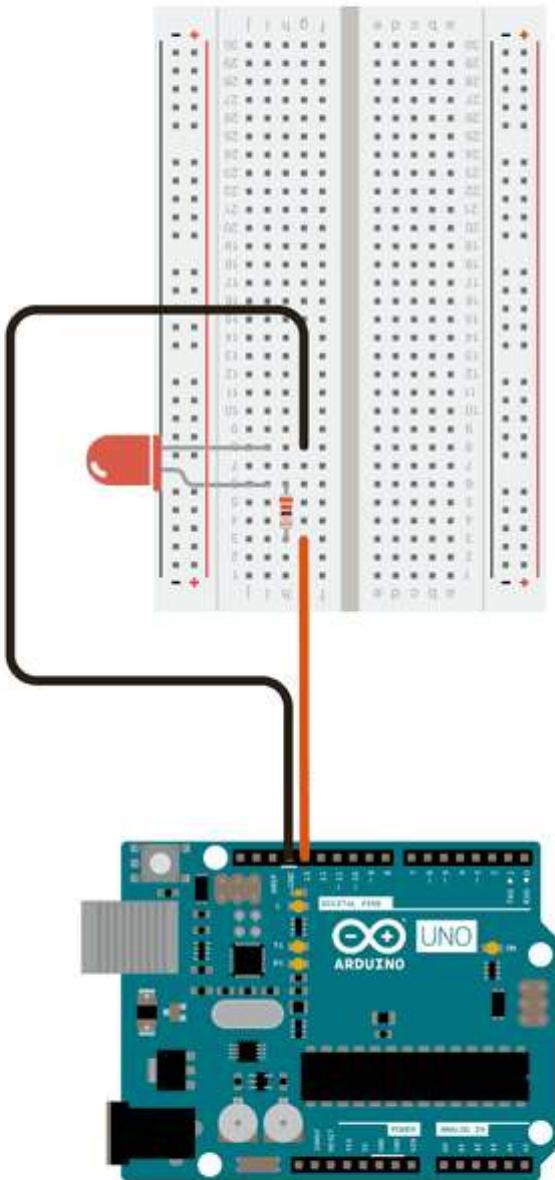
# Ohm's Law

Practical example: let's light up an LED. The arduino provides 5V  
What resistor value do we use?  $R = V / I \rightarrow R = 5V / 20mA$



# Ohm's Law

Practical example: let's light up an LED. The arduino provides 5V  
First, let's check the datasheet for the LED:

<https://learn.adafruit.com/all-about-leds/the-led-datasheet>

# Ohm's Law

We learnt that:

- Arduino provides 5V
- The LED has a running current of (about) 20mA
- The LED has a voltage drop of 1.8V
- The formula is:  $R = V / I$  ( $V = 3.2$ ,  $I = 20\text{mA}$ )

What numbers do we plug in?

# Ohm's Law

Well, we calculate the "remaining voltage":

$$V_{\text{remainder}} = V_{\text{in}} - V_{\text{drop}}$$

# Ohm's Law

Well, we calculate the “remaining voltage”:

$$V_{\text{remainder}} = V_{\text{in}} - V_{\text{drop}}$$

$$V_{\text{remainder}} = 5V - 1.8V = 3.2V$$

# Ohm's Law

Well, we calculate the "remaining voltage":

$$V_{\text{remainder}} = V_{\text{in}} - V_{\text{drop}}$$

$$V_{\text{remainder}} = 5V - 1.8V = 3.2V$$

We know the desired current: 20mA

# Ohm's Law

Well, we calculate the "remaining voltage":

$$V_{\text{remainder}} = V_{\text{in}} - V_{\text{drop}}$$

$$V_{\text{remainder}} = 5V - 1.8V = 3.2V$$

We know the desired current: 20mA

We apply the formula:  $R = V / I$

# Ohm's Law

Well, we calculate the "remaining voltage":

$$V_{\text{remainder}} = V_{\text{in}} - V_{\text{drop}}$$

$$V_{\text{remainder}} = 5V - 1.8V = 3.2V$$


We know the desired current: 20mA

We apply the formula:  $R = V / I$

$$R = 3.2V / 20mA = 160 \Omega$$

We will use 220  $\Omega$  (closest common value) or 330  $\Omega$  if we want it dimmer.

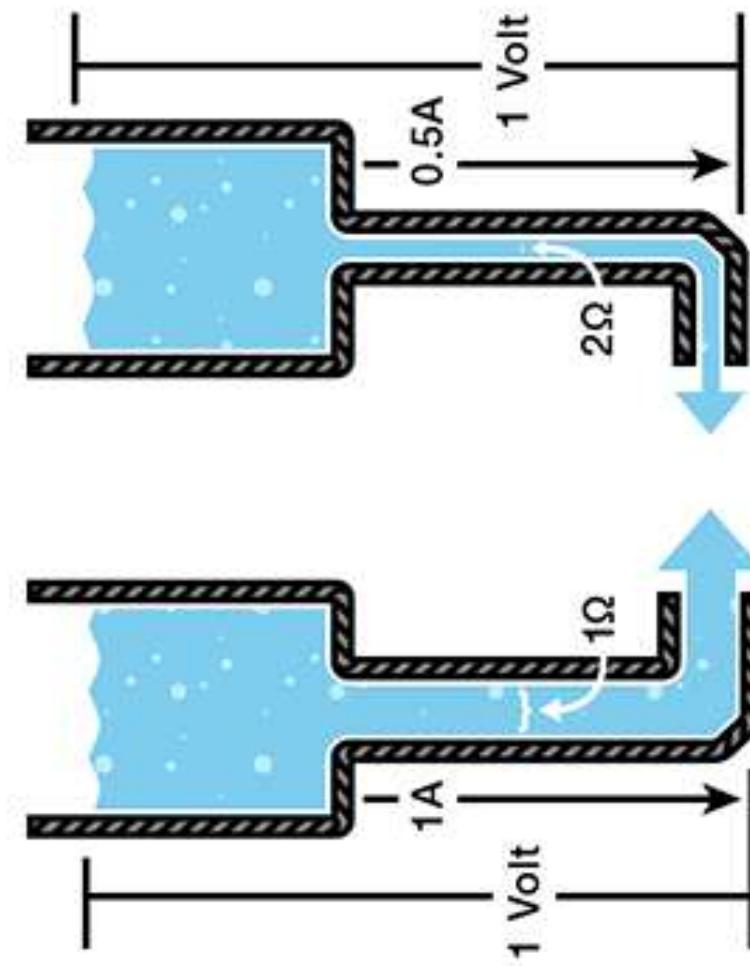
DC - maybe the difference makes more sense


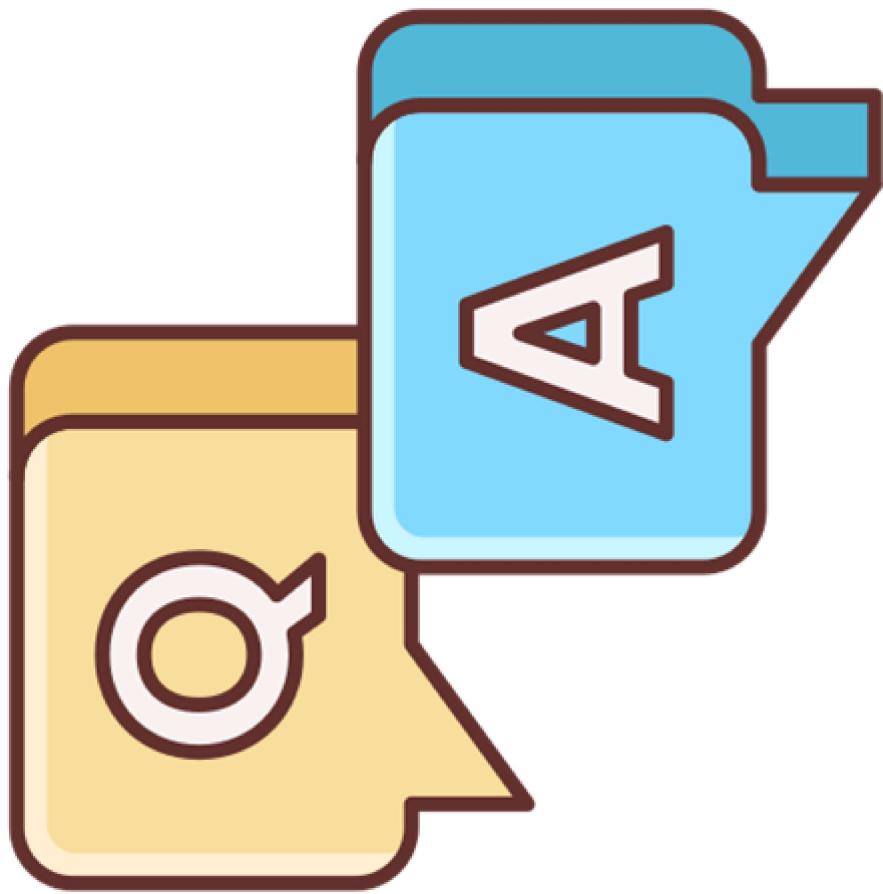
# Useful Links

- Electronics guide: <https://www.electronics-tutorials.ws>
- Simple electronics guide:
  - Voltage, Current and Resistance: [https://www.youtube.com/watch?v=OGa\\_b26eK2o](https://www.youtube.com/watch?v=OGa_b26eK2o)
  - Overview of Circuit Components: <https://www.youtube.com/watch?v=RHp04wKo8p>
  - Ohm's Law: <https://www.youtube.com/watch?v=lf0IMDZVwTl>
- Kirchoff's Law:
  - [KVL and KCL examples](#) (haven't watched it, but from the same series)
  - [KVL: https://www.youtube.com/watch?v=6Fr\\_mZ1nXFQ](https://www.youtube.com/watch?v=6Fr_mZ1nXFQ)
- [Series and parallel circuits](#) (long video)
- Super useful channel: [Basic electronics tutorials](#) ([list](#))
- [Resistor before or after LED?](#)
- [How to use a breadboard](#)
- [How to calculate correct resistor for LEDs](#)
- [Detailed overview or resistors](#) (pretty cool video)

Just use google, though. Each year I find resources that are better and better.



[Source](#)

# Attendance check

